

# LSV PA#1 Report

B07901056 張凱鈞

## Part 1.

### (b) 3. Logic network

Network structure visualized by ABC  
Benchmark "4numserialadder". Time was Mon Oct 4 16:38:40 2021.

The network contains 10 logic nodes and 3 latches.

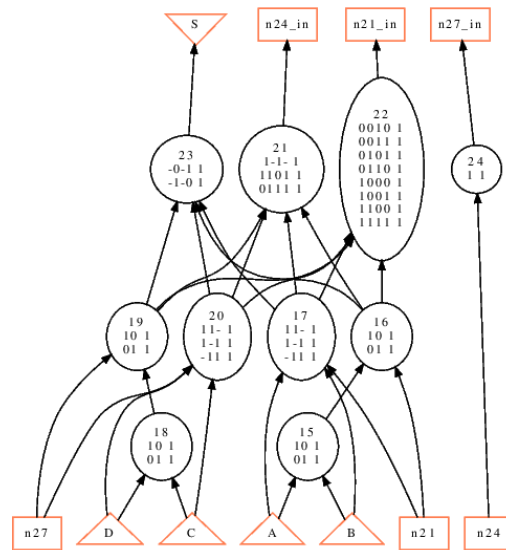


Fig. 1-1 Logic Network

## 5. AIG

Network structure visualized by ABC  
Benchmark "4numserialadder". Time was Mon Oct 4 16:47:16 2021.

The network contains 44 logic nodes and 3 latches.

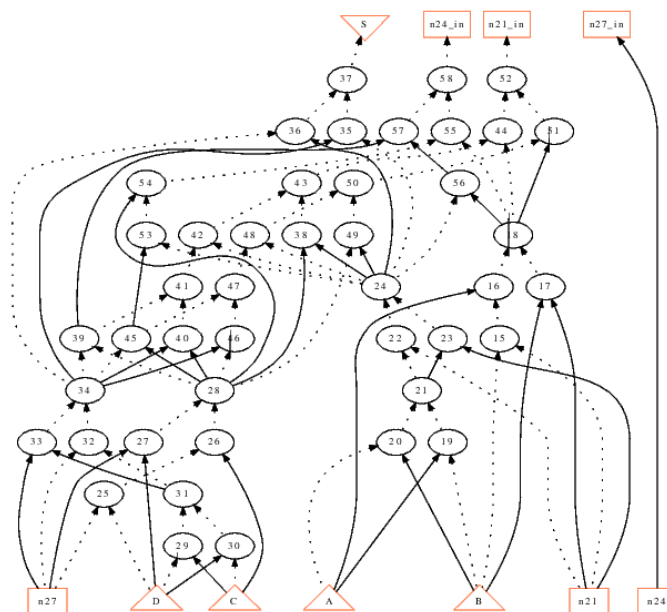


Fig. 1-2 AIG

## 7. BDD

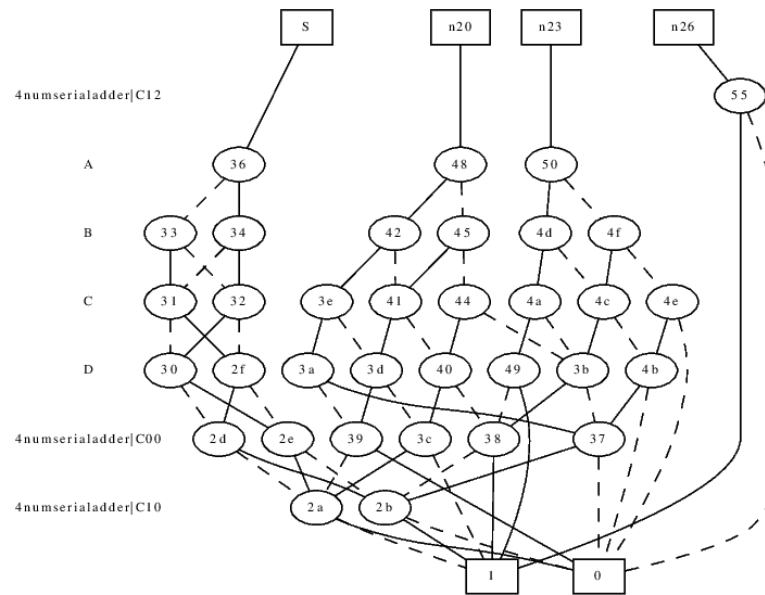


Fig. 1-3 BDD

### Part 2.

- (a) 1. As the following figures show, the command “aig” only changes the representation of local functions into AIG form (Fig. 2-2), while the command “strash” converts the whole network into a structurally hashed AIG (Fig. 1-2).

```
abc 09> read lsv_fall_2021/pal/adder.blif
Hierarchy reader flattened 3 instances of logic boxes and left 0 black boxes.
abc 10> aig
abc 10> print_stats
4numserialadder          : i/o = 4/ 1 lat = 3 nd = 10 edge = 27 aig = 46 lev = 3
abc 10> strash
abc 11> print_stats
4numserialadder          : i/o = 4/ 1 lat = 3 and = 44 lev = 10
```

Fig. 2-1 The whole network becomes AIG after “strash” (only AND gates), while “aig” only changes local function representation

Network structure visualized by ABC  
Benchmark “4numserialadder”. Time was Mon Oct 4 17:24:57 2021.

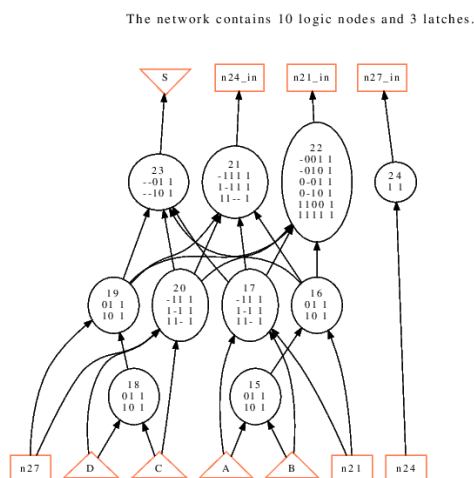


Fig. 2-2 The logic network after command “aig”/“bdd” and “show”

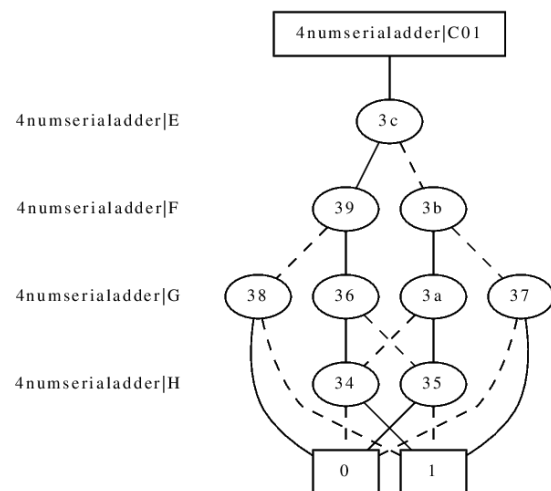


Fig. 2-3 The BDD representation of the node n22 (by “show\_bdd n22”)

2. Similarly, the command “*bdd*” only changes the representation of local functions into BDD form (Fig. 2-2, Fig. 2-3), while the command “*collapse*” converts the whole network into a BDD (Fig. 1-3).

```
abc 01> read lsv_fall_2021/pal/adder.blif
Hierarchy reader flattened 3 instances of logic boxes and left 0 black boxes.
abc 02> bdd
abc 02> print_stats
4numserialadder          : i/o =    4/    1 lat =    3 nd =   10 edge =   27 bdd =   30 lev = 3
abc 02> collapse
abc 03> print_stats
4numserialadder          : i/o =    4/    1 lat =    3 nd =    4 edge =   19 bdd =   28 lev = 1
```

Fig. 2-4 It's shown that the network structure after “*collapse*” is different with the structure after “*bdd*”

(b) Use “*renode*” to convert the AIG into a logic network first, then use “*sop*” to change node function expression into SOP form.

```
abc 04> read lsv_fall_2021/pal/adder.blif
Hierarchy reader flattened 3 instances of logic boxes and left 0 black boxes.
abc 05> strash
abc 06> print_stats
4numserialadder          : i/o =    4/    1 lat =    3 and =   44 lev = 10
abc 06> renode
abc 07> print_stats
4numserialadder          : i/o =    4/    1 lat =    3 nd =   21 edge =   45 aig =   42 lev = 6
abc 07> sop
abc 07> print_stats
4numserialadder          : i/o =    4/    1 lat =    3 nd =   21 edge =   45 cube =   32 lev = 6
```

Fig. 2-5