

# Logic Synthesis & Verification, Fall 2023

National Taiwan University

## Programming Assignment 1

Name: 陳均豪

Id: r12k41016

### Problem 2. [Using ABC]

*Solution:*

- (a) two-bit unsigned multiplier  $Y = A * B$ , where  $A = (a_1 a_0)$  and  $B = (b_1 b_0)$  are two-bit unsigned integers, and  $Y = (y_3 y_2 y_1 y_0)$  is a four-bit unsigned integer. We can find,

$$\begin{array}{r} \begin{array}{cc} & a_1 & a_0 \\ * & b_1 & b_0 \\ \hline & a_1 * b_0 & a_0 * b_0 \\ a_1 * b_1 & a_0 * b_1 & \\ \hline c_2 & a_1 * b_1 + c_1 & a_1 * b_0 + a_0 * b_1 & a_0 * b_0 \end{array} \end{array}$$

Then, we can easily write the blif with the following formula,

$$\left\{ \begin{array}{l} y_0 = a_0 \wedge b_0 \\ y_1 = (a_0 \wedge b_1) \oplus (a_1 \wedge b_0) \\ y_2 = (a_1 \wedge b_1) \oplus ((a_0 \wedge b_1) \wedge (a_1 \wedge b_0)) \\ y_3 = (a_1 \wedge b_1) \wedge ((a_0 \wedge b_1) \wedge (a_1 \wedge b_0)) \end{array} \right.$$

Or, we can write down the truth table to construct the blif

a1	a0	b1	b0	y3	y2	y1	y0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

(b) 1. read mul.blif


```
abc 01> read mul.blif
```

2. print\_stats

```
abc 02> print_stats
mul          : i/o = 4/ 4 lat = 0 nd = 4 edge = 14 cube = 8 lev = 1
```

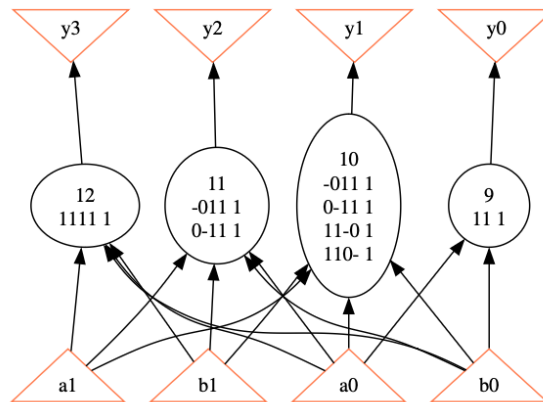3. show

The network contains 4 logic nodes and 0 latches.




4. strash

```
abc 02> strash
```

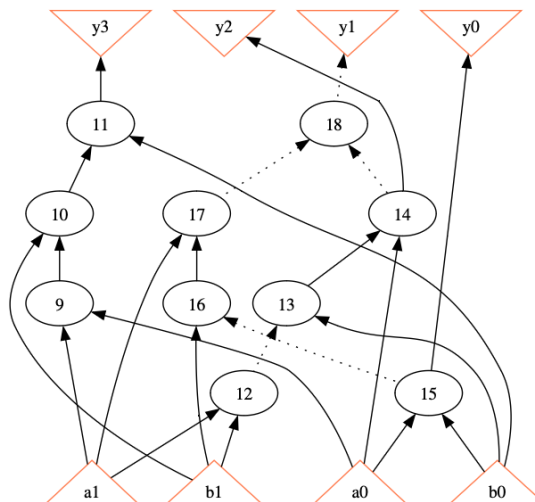5. show


The network contains 10 logic nodes and 0 latches.



## 6. collapse

```
abc 03> collapse
```

## 7. show\_bdd -g

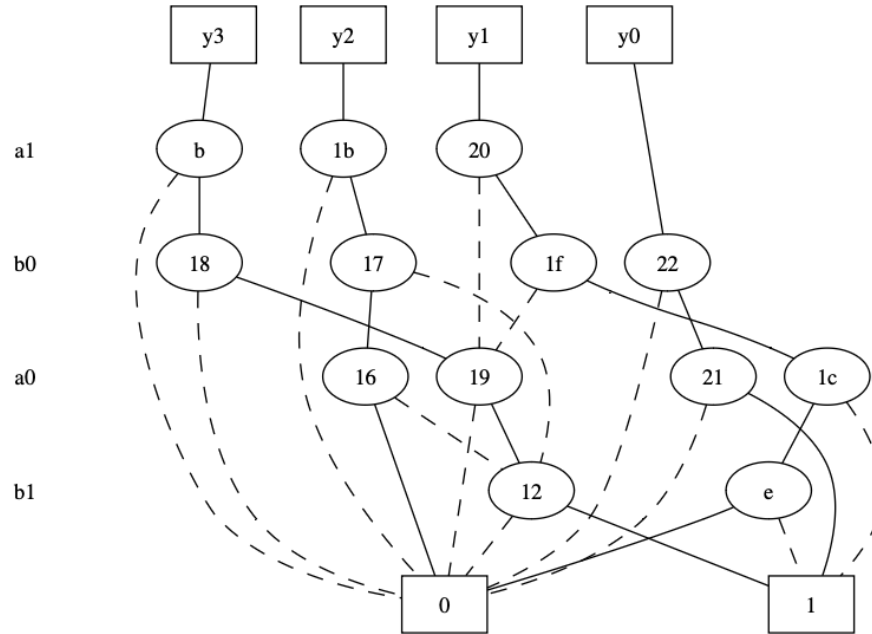


◇

### Problem 3. [ABC Boolean Function Representations]

*Solution:*

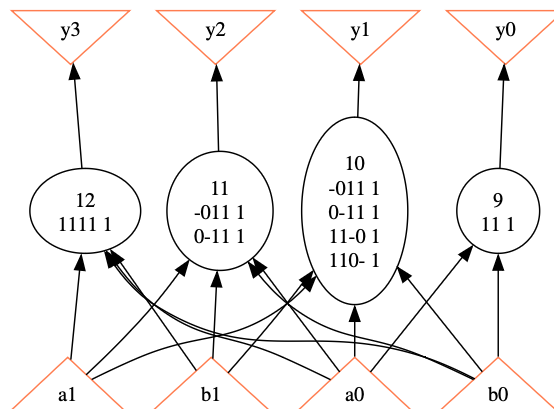
- (a) 1. Command **"aig"**

The network contains 4 logic nodes and 0 latches.


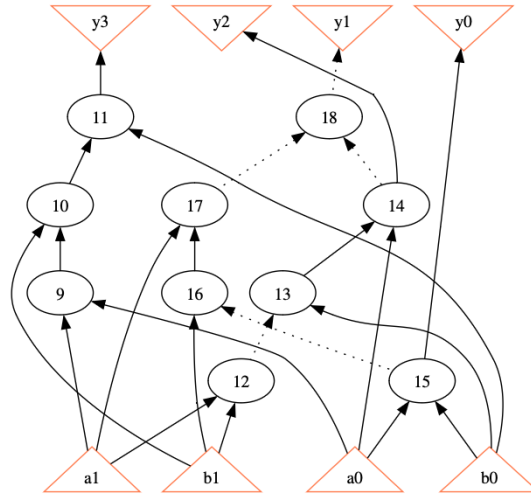
## Command "strash"


The network contains 10 logic nodes and 0 latches.



We can see that the figure that **ABC** shows has a different representation. The main difference is that in the command **show** (src/base/abc/abcShow.c:292), it will convert the logic network into "SOP" form to show the network, and **AIG** is the type of logic network, but the **Strashed AIG** is not the logic network in the definition in the ABC.

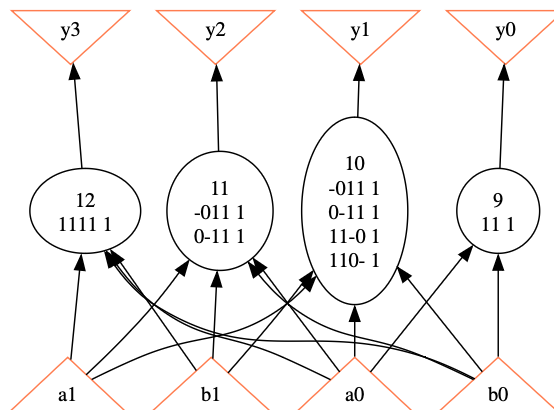
## 2. Command "bdd"

The network contains 4 logic nodes and 0 latches.


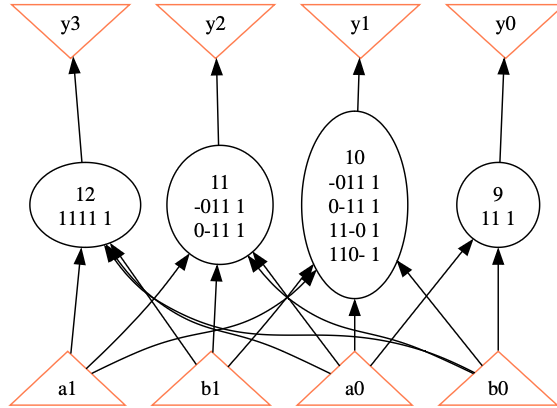
## Command "collapse"

The network contains 4 logic nodes and 0 latches.




The command "bdd" and command "collapse" have the same representation because they are both logic networks. Therefore, the command **show** will convert them into the same "SOP" form to show the network.

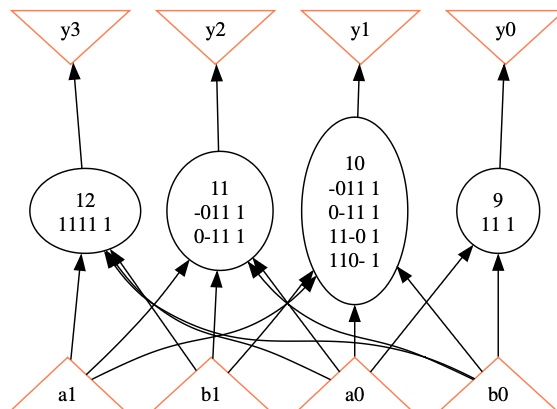- (b) After we get the structurally hashed AIG, we need to convert it into logic network first, using the command **"logic"**. Then, we can use the command **"collapse"** to obtain the same result as the previous result. Finally, we can use the command **"sop"** to convert a network into SOP form.

```
abc 01> read mul.blif
abc 02> strash
abc 03> logic
abc 04> collapse
abc 05> sop
abc 05> show
```

The network contains 4 logic nodes and 0 latches.



◇