

LSV PA1 B07901020 劉昀昇

Part A

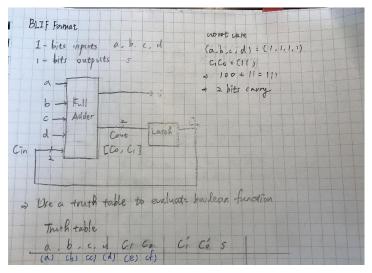


Network structure visualized by ABC Benchmark "4numbersadder". Time was Thu Oct 7 16:18:31 2021.

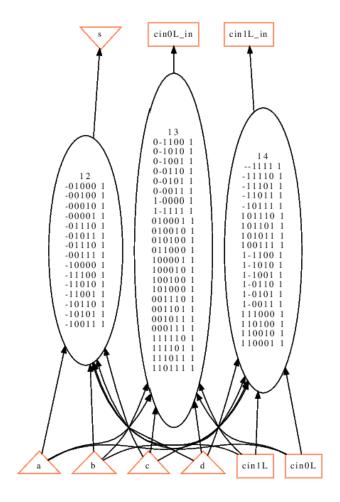
The network contains 3 logic nodes and 2 latches.



After strash

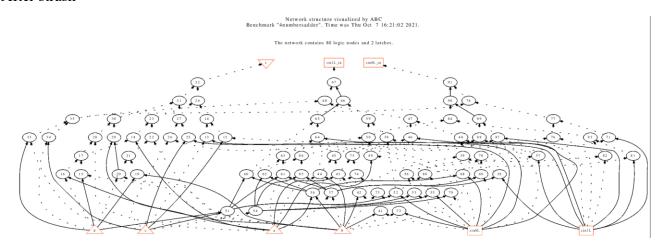

show bdd-g

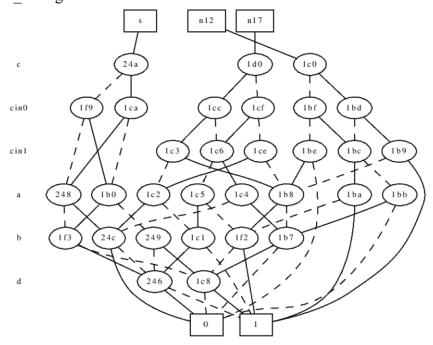

Part B

- (a) Compare the following differences with the four-number serial adder example.
 - logic network in AIG (by command aig) vs. structurally hashed AIG (by command strash) AIG: Converts local functions of the nodes to AIGs, relation between nodes are unchanged, node structure remains.


Strash: Convert global network to AIGs by one-level structural hashing, nodes structure is no longer maintained

```
abc 25> read lsv_fall_2021/pa1/4numbersadder.blif
abc 26> aig
abc 26> print_stats
4numbersadder : i/o = 4/ 1 lat = 2 nd = 3 edge = 18 aig = 1
91 lev = 1

abc 28> read lsv_fall_2021/pa1/4numbersadder.blif
abc 29> strash
abc 30> print_stats
4numbersadder : i/o = 4/ 1 lat = 2 and = 80 lev = 8
```

• logic network in BDD (by command bdd) vs. collapsed BDD (by command collapse) bdd: Converts local functions of the nodes to BDDs. (nodes number remained unchanged, level unchanged)

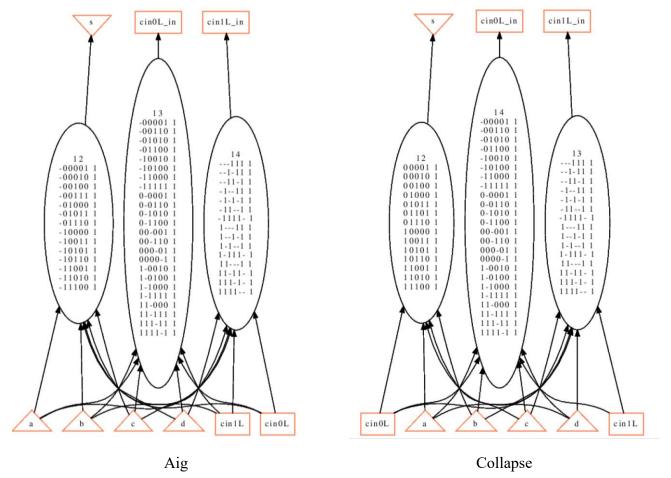Collapse: Recursively composes the fanin nodes into the fanout nodes resulting in a network, it is built by global BDDs (level changed because each CO is composed by a node whose fanins are CIs, here because original circuit is one-level already, so differences are minor. However, some differences can be observed from command print_stats)



(b) Given a structurally hashed AIG, find a sequence of ABC command(s) to convert it to a logic network with node function expressed in sum-of-products (SOP).

BDD based SOP generation: collapse + sop

```
abc 11> read lsv_fall_2021/pa1/4numbersadder.blif
abc 12> strash
abc 13> collapse
abc 14> sop
abc 14> print_stats
4numbersadder : i/o = 4/ 1 lat = 2 nd = 3 edge = 17 cube =
53 lev = 1
```

SAT based SOP generation: satclp

```
08> read lsv_fall_2021/pa1/4numbersadder.blif
abc 09> strash
abc 10> print_stats
                                : i/o =
                                            4/
                                                  1 lat =
                                                               2 and =
                                                                             80 lev = 8
4numbersadder
abc 10> satclp
abc 11> print stats
4numbersadder
                                : i/o =
                                                  1 lat =
                                                                                           17 cube =
                                            4/
                                                               2 nd =
                                                                            3 edge =
```