
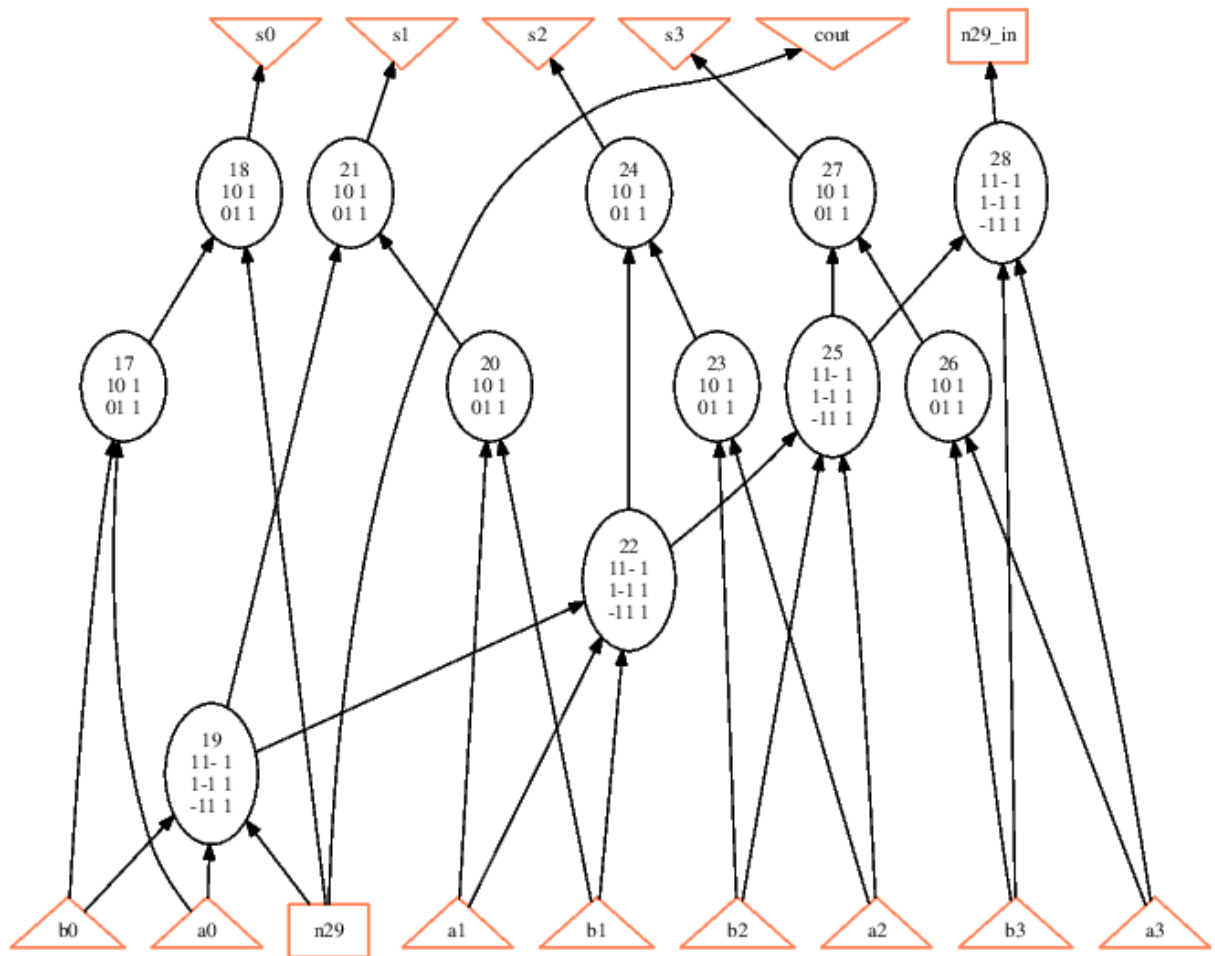


Network structure visualized by ABC
Benchmark "ser_adder". Time was Sat Oct 2 21:32:19 2021.

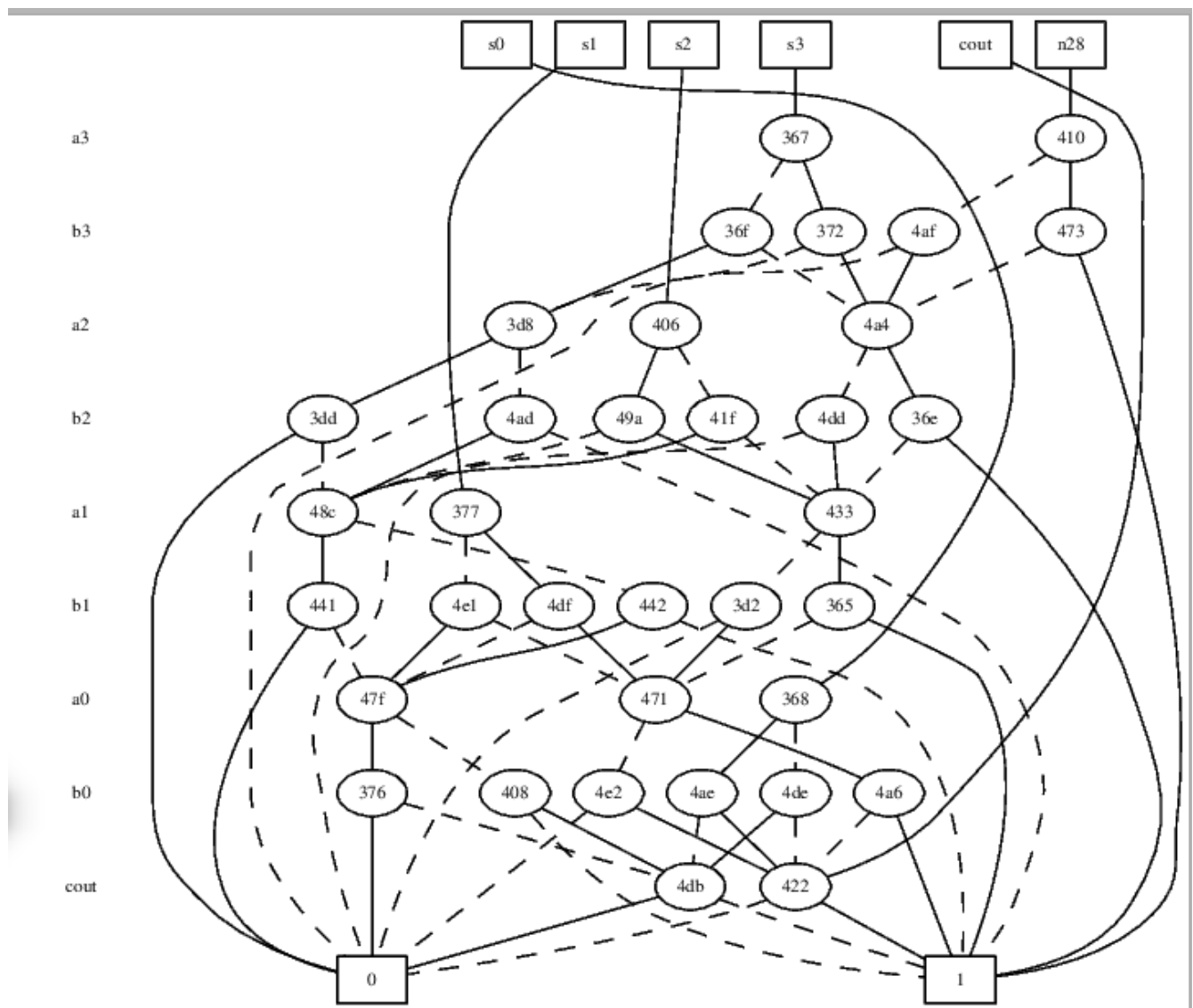The network contains 12 logic nodes and 1 latches.




Logic Network



BDD, using collapsed

Network structure visualized by ABC
Benchmark "ser_adder". Time was Sat Oct 2 21:33:23 2021.

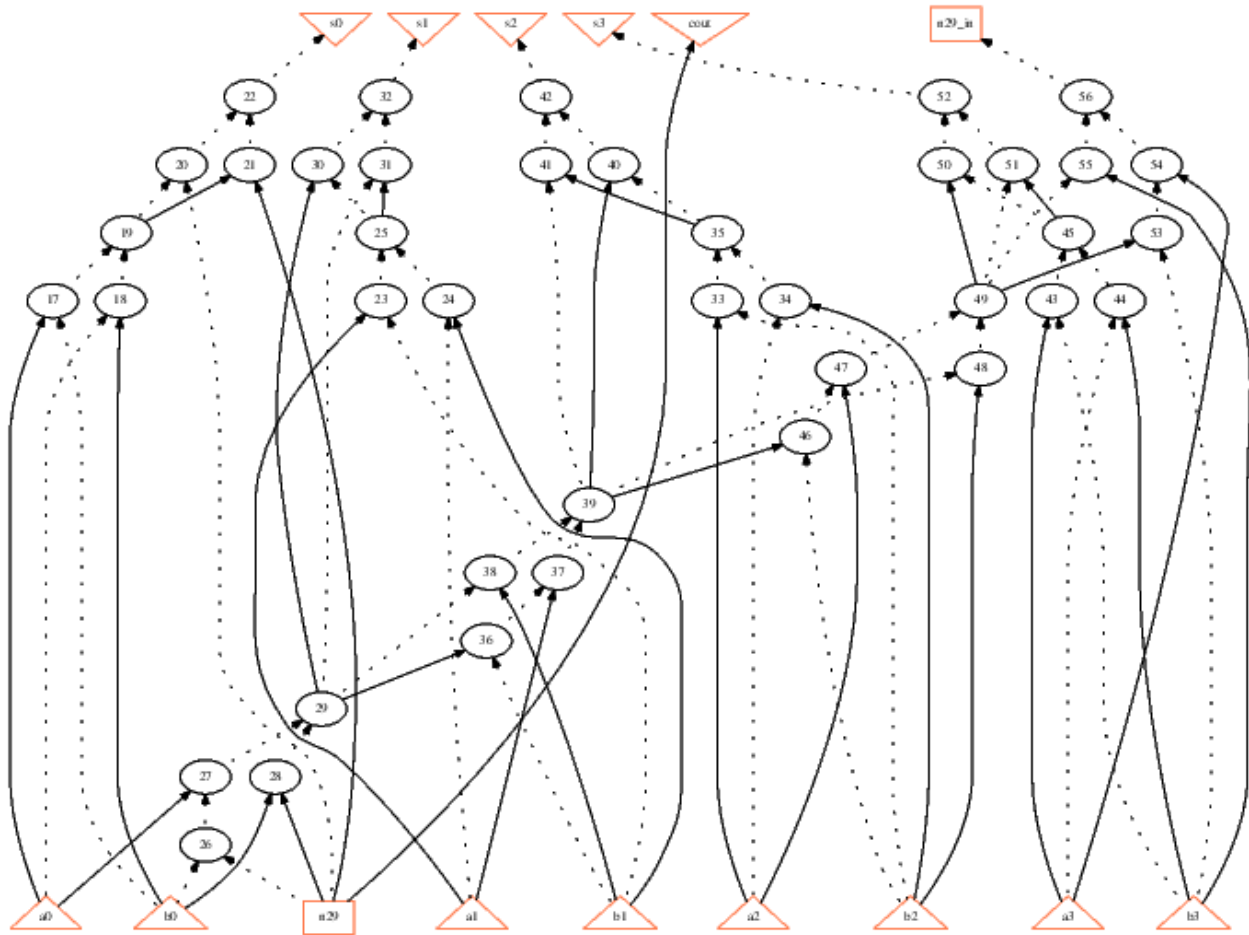The network contains 40 logic nodes and 1 latches.



aig

(1) logic network in AIG (by command `aig`) vs. structurally hashed AIG (by command `strash`)

`aig` command convert the local function node in logic network to aig

`strash` command convert the global function into a aig

(2) logic network in BDD (by command `bdd`) vs. collapsed BDD (by command `collapse`)

`bdd` command convert the local function node in logic network to bdd

`collapse` command build the global bdd for global function

(3) Given a structurally hashed AIG, find a sequence of ABC command(s) to covert it to a logic network with node function expressed in sum-of-products (SOP)

using command `$logic`