

1. 一頁一張 visualize the network structure:

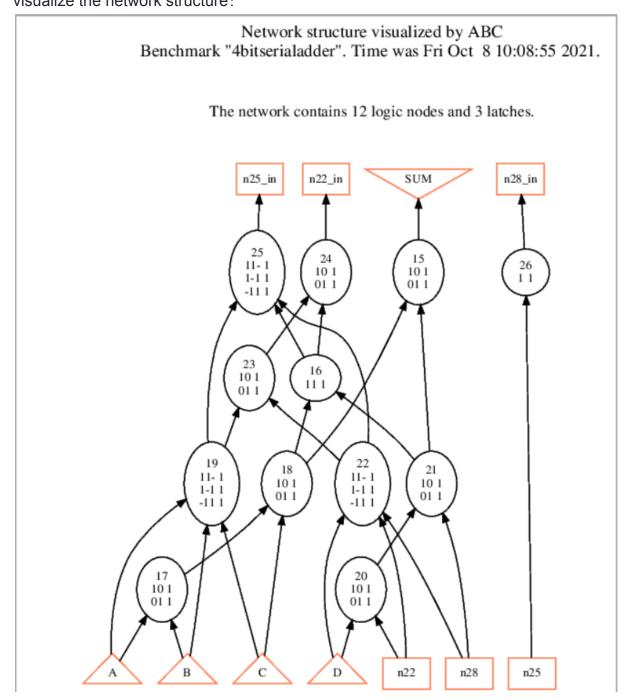


visualize the AIG:

Network structure visualized by ABC Benchmark "4bitserialadder". Time was Fri Oct 8 10:12:48 2021.

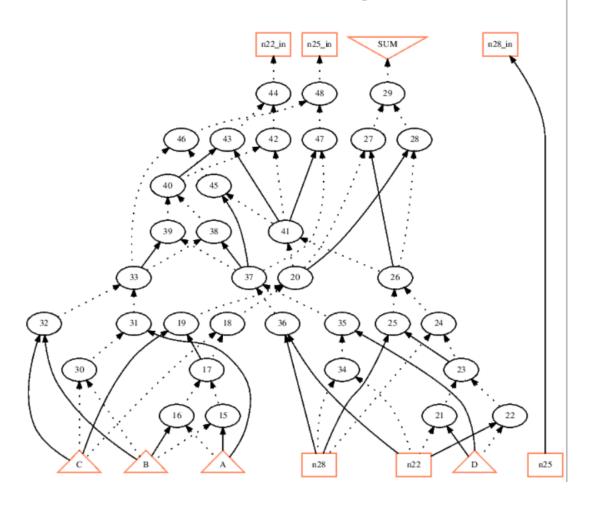The network contains 34 logic nodes and 3 latches.



visualize the BDD:

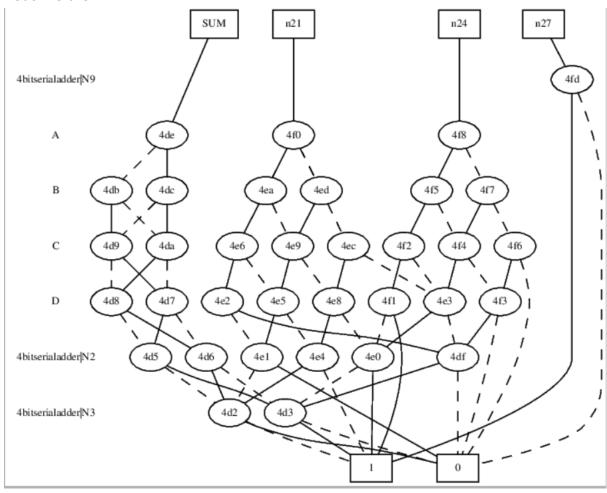

- 2.
- (a) Compare the following differences with the four-bit adder example.
 - (1) logic network in AIG (by command aig) vs. structurally hashed AIG (by command strash)

```
abc 02> aig
abc 02> print_stats
4bitserialadder : i/o = 4/ 1 lat = 3 nd = 12 edge = 26 aig = 34 lev = 4
```

aig 的功能是將原本的 logic network 裡面的 gates 都變成 and-inv 的形式

```
abc 02> strash
abc 03> show
abc 03> Warning: Missing charsets in String to FontSet conversion
abc 03> print_stats
4bitserialadder : i/o = 4/ 1 lat = 3 and = 34 lev = 8
```

strash的功能則是直接用 AIG graph 代表整個 logic network

雖然兩者的功能都是把 logic network 化成 AIG, 但 aig 應該只是把原本的SOP給拆開來(所以依然還是SOP的狀態, 改變的只有node function), 但 strash 則是把原本的 logic network 轉換成由 POs 連到 PIs 的 AIG

(2) logic network in BDD (by command bdd) vs. collapsed BDD (by command collapse)

```
abc 02> bdd
abc 02> show
abc 02> warning: Missing charsets in String to FontSet conversion

abc 02> print_stats
4bitserialadder : i/o = 4/ 1 lat = 3 nd = 12 edge = 26 bdd = 28 lev = 4
abc 02>
abc 02>
abc 02>
abc 02>
abc 02> collapse
abc 03> print_stats
4bitserialadder : i/o = 4/ 1 lat = 3 nd = 4 edge = 19 bdd = 28 lev = 1
```


bdd 的功能是將 logic network 用 BDD 的表示方式存起來

collapse的功能是把整個logic network改成用一個 level 表示

下頁的圖可以看到collapse之後再用show而非show_bdd的結果,可以發現它會把整個logic network變成一個SOP

Network structure visualized by ABC Benchmark "4bitserialadder". Time was Fri Oct 8 10:40:49 2021.

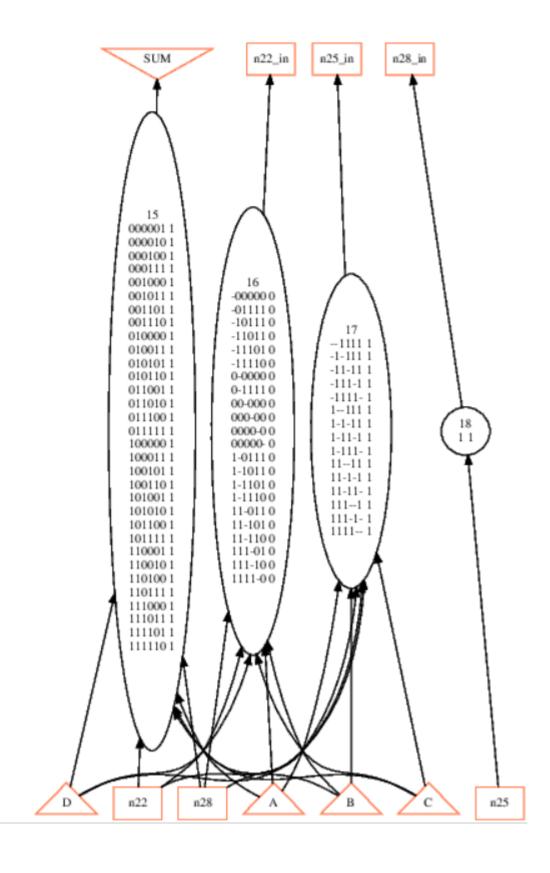The network contains 4 logic nodes and 3 latches.



(b) Given a structurally hashed AIG, find a sequence of ABC command(s) to covert it to a logic network with node function expressed in sum-of-products (SOP).

>logic (就一個)