

LSV Programming Assignment #1

b07901135 EE4 何國瑋

2021-10-08

1 Part 1

Network structure visualized by ABC
Benchmark "adder4s". Time was Fri Oct 8 00:33:07 2021.

The network contains 14 logic nodes and 3 latches.

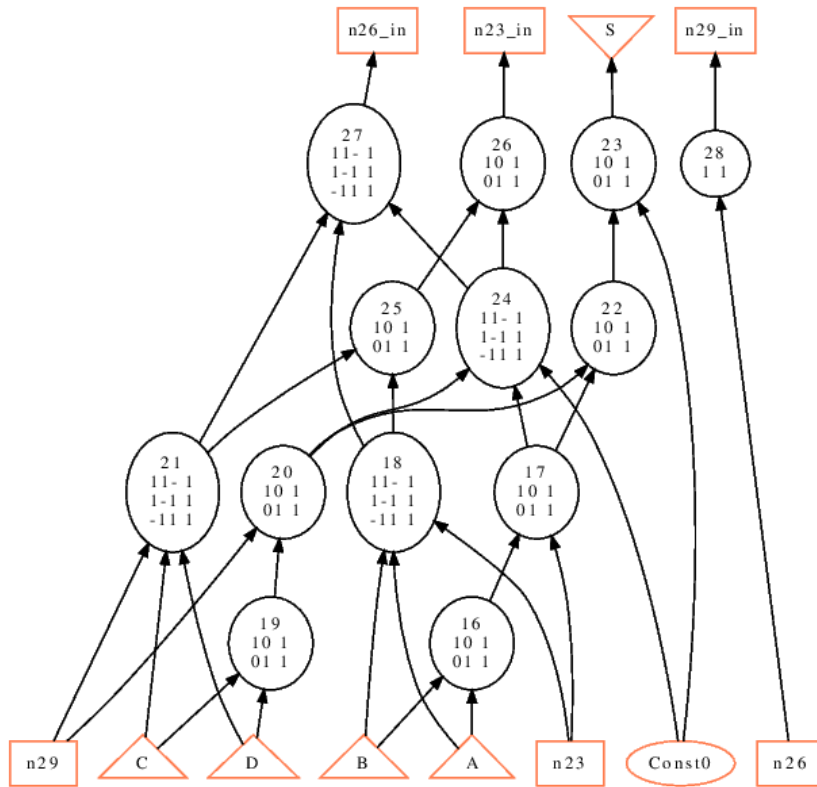


Figure 1: Original network

The network contains 34 logic nodes and 3 latches.

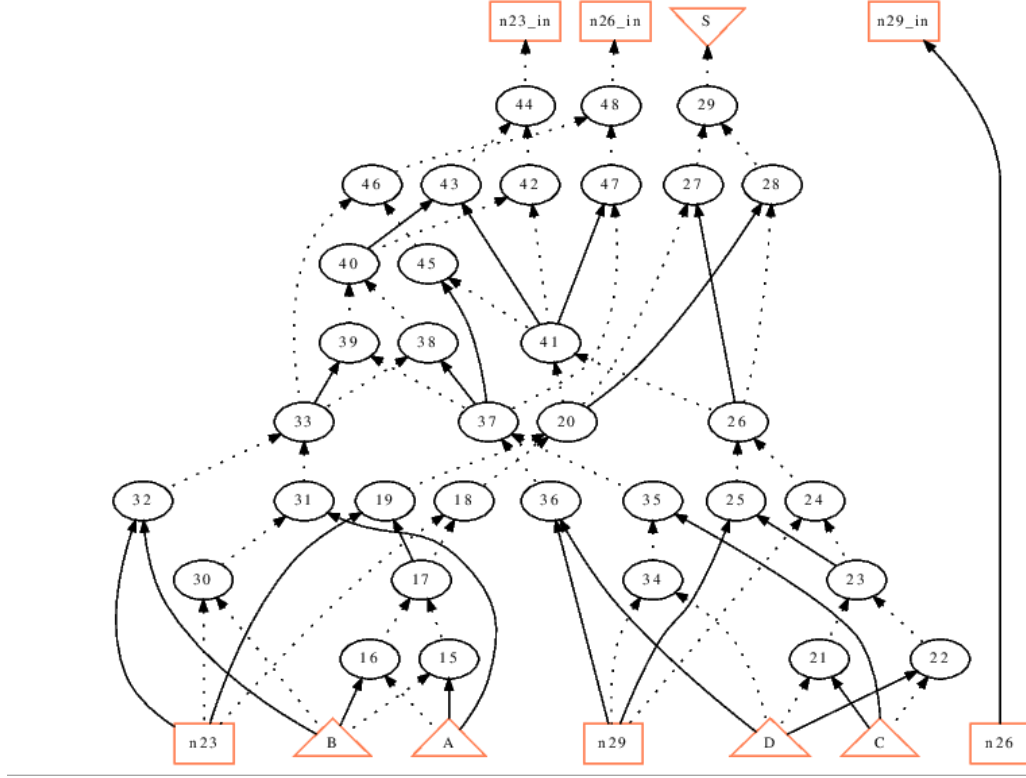


Figure 2: Strashed network

2 Part 2

(a) The difference between:

1. logic network in AIG (by command **aig**) vs. structurally hashed AIG (by command **strash**)

The command **aig** only converts the local functions of each nodes into AIG. The nodes in the network remain the same. After the command, the command **show** will show the exact same network, but the command **print_stats** will show the number of aig nodes.

The command **strash** structurally hash the whole network and turn it into AIG.

2. logic network in BDD (by command **bdd**) vs. collapsed BDD (by command **collapse**)

The command **bdd** only converts the local function of each nodes into BDD. The command **show_bdd** can show the bdd of each PO.

The command **collapse** collapses the network, resulting in one node for each PO, whose fanins are all PIs. A global BDD is built and showing the BDD of a single PO is not available.

(b) The command **logic** transforms the AIG into a logic network with the SOP representation of the two-input AND-gates.

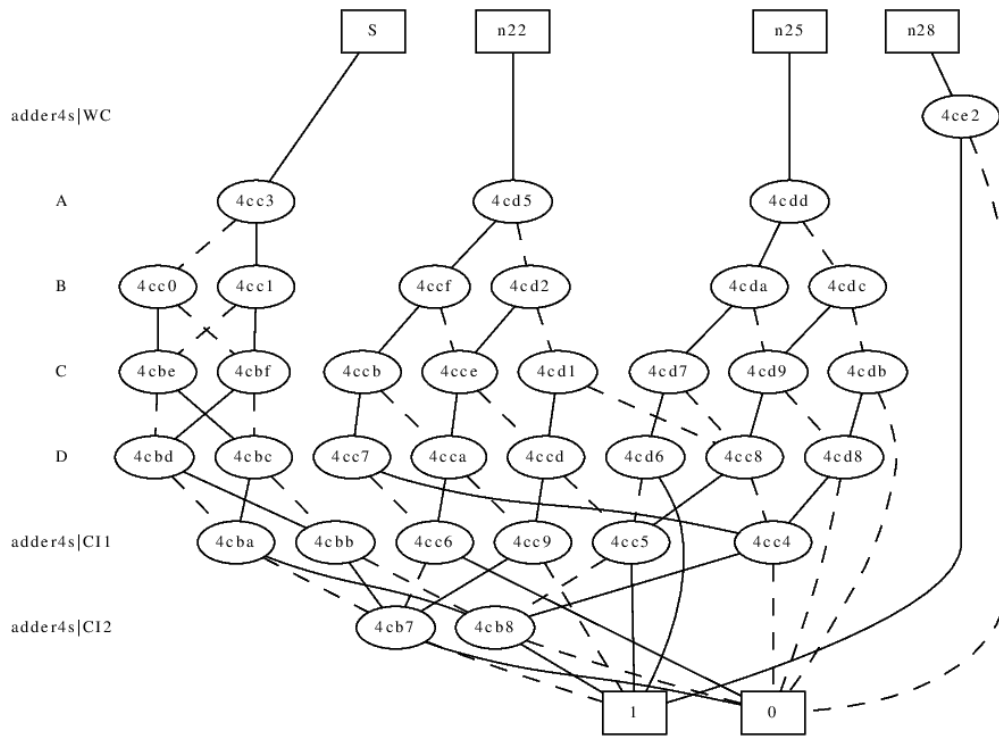


Figure 3: BDD of flattened network