


2.(b)

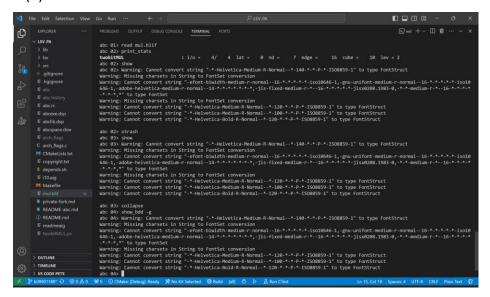


3.

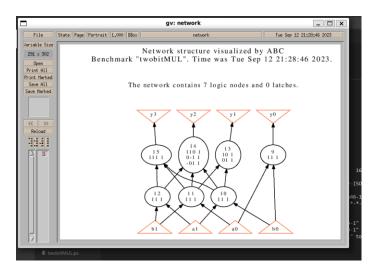

5.

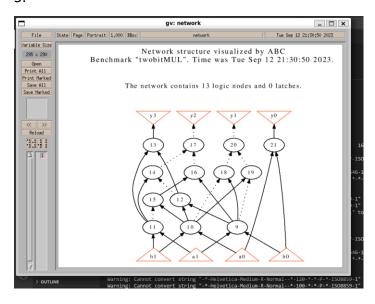

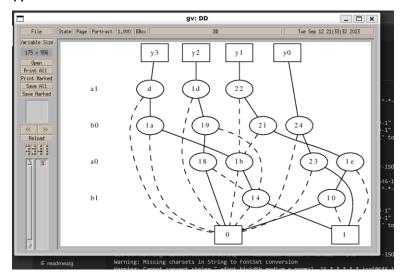

3.(a)

1.


After command "aig", the network structure shown by command "show" is as same as the original one. However, the structure in each internal node is now constructed by aig ("print stats" shows that it has 14 aig).

As for command "strash", the network structure shown by command "show" is different, each node in the graph is an and gate and each edge represents a positive or negative value of the fanin.

Logic network in AIG (by command "aig")

Network structure visualized by ABC Benchmark "twobitMUL". Time was Tue Sep 12 22:00:55 2023.

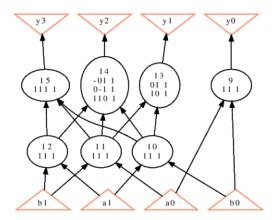
The network contains 7 logic nodes and 0 latches.



structurally hashed AIG (by command "strash")

```
abc 02> strash
abc 03> print_stats
twobitMUL : i/o = 4/ 4 lat = 0 and = 13 lev = 4
abc 03> show
abc 03> Warning: Cannot convert string "-*-Helvetica-Medium-R-Normal--*-140-*-*-P-*-ISO8859-1" to type FontStruct
Warning: Missing charsets in String to FontSet conversion
Warning: Cannot convert string "-efont-biwidth-medium-r-normal--16-*-*-*--iso10646-1,-gnu-unifont-medium-r-normal--16-*-*-*-iso10646-1,-adobe-helvetica-medium-r-normal--14-*-*-*-*,-jis-fixed-medium-r-*--16-*-*-*-jisx0208.1983-0,-*-*-medium-r-*--16-*-*-*
Warning: Missing charsets in String to FontSet conversion
Warning: Cannot convert string "-*-Helvetica-Medium-R-Normal---*-120-*-*-P-*-ISO8859-1" to type FontStruct
Warning: Cannot convert string "-*-Helvetica-Medium-R-Normal---*-120-*-*-P-*-ISO8859-1" to type FontStruct
Warning: Cannot convert string "-*-Helvetica-Bold-R-Normal---*-120-*-*-P-*-ISO8859-1" to type FontStruct
```

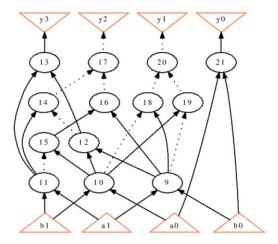The network contains 13 logic nodes and 0 latches.




2.


Both command "bdd" and "collapse" generate the same bdd graph. However, command "bdd" won't change the result of the command "show", it only changes the structure of the internal node. On the other hand, command "collapse" makes the network structure shown by "show" different. Also, the results shown by command "print_stats" are different for these two commands. For example, the number of bdd is 16 and 14 respectively.

logic network in BDD (by command "bdd")

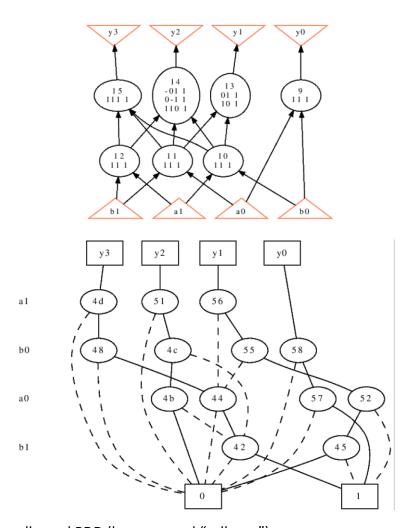The network contains 7 logic nodes and 0 latches.




collapsed BDD (by command "collapse")

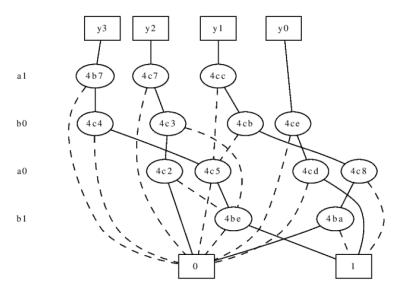

Network structure visualized by ABC Benchmark "twobitMUL". Time was Tue Sep 12 22:14:37 2023.

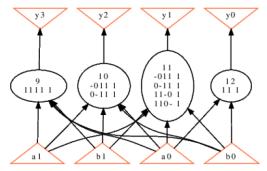The network contains 4 logic nodes and 0 latches.



3.(b) First, read mul.blif Second, strash Third, renode Last, sop

Network structure visualized by ABC Benchmark "twobitMUL". Time was Wed Sep 13 20:40:52 2023.

The network contains 10 logic nodes and 0 latches.

