


HW1

1.

After step3


Network structure visualized by ABC
Benchmark "serial_adder". Time was Thu Oct 7 21:35:24 2021.

 The network contains 10 logic nodes and 2 latches.




After step5

 The network contains 9 logic nodes and 2 latches.



After step7

 

2.

(a)

Strash vs aig

```
abc 02> print_stats
serial_adder          : i/o =   4/   1 lat =   2 nd =   10 edge =   20 aig =   66 lev = 3
abc 02> strash
abc 03> print_stats
serial_adder          : i/o =   4/   1 lat =   2 and =    9 lev = 4
abc 03> 
```

aig : Converts **local** functions of the nodes to AIGs.

strash: Transforms the current network into an AIG by one-level structural hashing. The resulting AIG is a logic network composed of two-input AND gates and inverters represented as complemented attributes on the edges. Structural hashing is a purely combinational transformation, which does not modify the number and positions of latches.

(One-level strashing: When a new AND-gate is added, checks is performed for a node with the same fanins (up to permutation of gate inputs).)


The number of gates and levels are different, while the number of latches remains the same.

bdd vs collapse

```
abc 02> print_stats
serial_adder          : i/o = 4/ 1 lat = 2 nd = 10 edge
= 20 bdd = 35 lev = 3
abc 02> collapse
abc 03> print_stats
serial_adder          : i/o = 4/ 1 lat = 2 nd = 3 edge
= 4 bdd = 4 lev = 1
abc 03>
```

bdd : Converts **local** functions of the nodes to BDD.

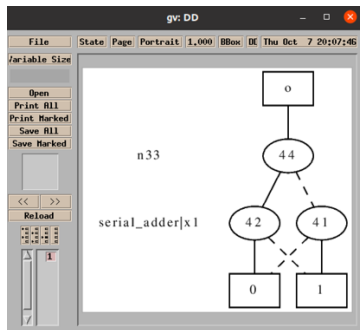Ex: Single logic node x1 converted to BDD.



collapse : Recursively composes the fanin nodes into the fanout nodes resulting in a network, in which each CO is produced by a node, whose fanins are CIs. Collapsing is performed by building **global** functions using BDDs and is, therefore, limited to relatively small circuits. After collapsing, the node functions are represented using BDDs.

(b)

renode , sop.