
lsv report pa1 problem 2,3 r11943107 賴君皓

network structure:

Network structure visualized by ABC Benchmark "mul". Time was Sun Sep 17 00:54:28 2023.

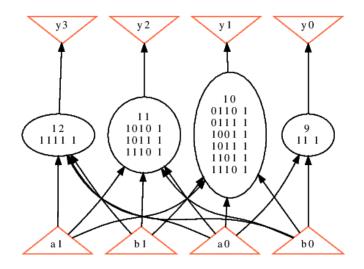
The network contains 4 logic nodes and 0 latches.




AIG:

Network structure visualized by ABC Benchmark "mul". Time was Sun Sep 17 00:55:33 2023.

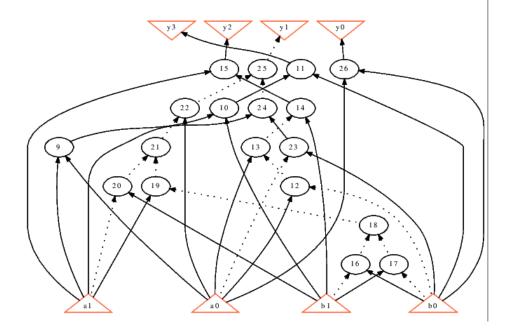The network contains 18 logic nodes and 0 latches.



BDD:

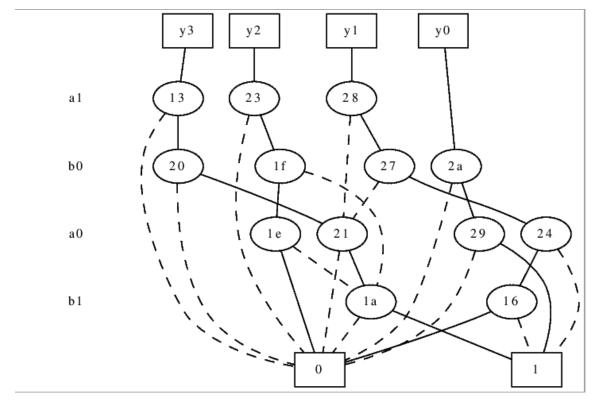

3 (a)

> "AIG" is the original and-inverter graph, and the "strash" make it simpler and smaller using structural hashing technique. With the strash command we can save some memory.

```
abc 05> read mul.blif
abc 06> aig
abc 06> print_stats
mul : i/o = 4/ 4 lat = 0 nd = 4 edge = 14 aig = 18 lev = 1
abc 06> strash
abc 07> print_stats
mul : i/o = 4/ 4 lat = 0 and = 18 lev = 6
```

2. It is the same idea with "strash" to "AIG". "Collapse" use recursive composing technique to make the node number less, so system memory could be saved.

```
abc 07> read mul.blinabc 08> bdd
abc 08> print_stats
                                                                                                         17 lev = 1
mul
                                : i/o =
                                           4/
                                                     lat =
                                                                 nd =
                                                                             edge =
                                                                                              bdd
abc 08> collapse
abc 09> print_stats
                                : i/o =
                                                  4 lat =
                                                              0 nd =
                                                                           4 edge =
                                                                                          14 bdd
                                                                                                         14 lev = 1
```

```
abc 04> read mul.blif
abc 05> sop
abc 05> show
```

Network structure visualized by ABC Benchmark "mul". Time was Sun Sep 17 01:07:32 2023.

The network contains 4 logic nodes and 0 latches.

