

Department of Electrical Engineering, National Taiwan University

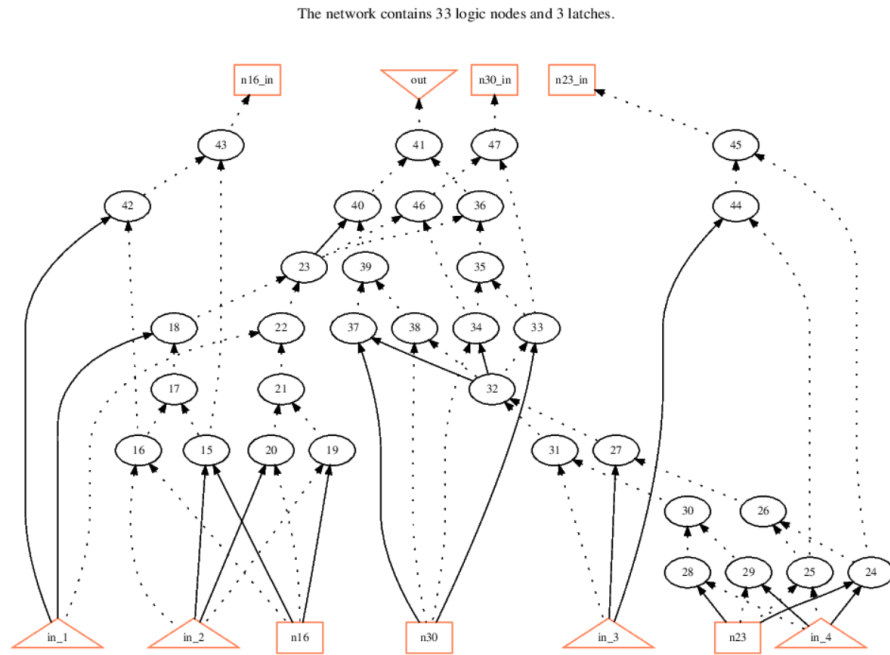


Figure 2: Step 5

2.(b)

One single command `logic` suffices.

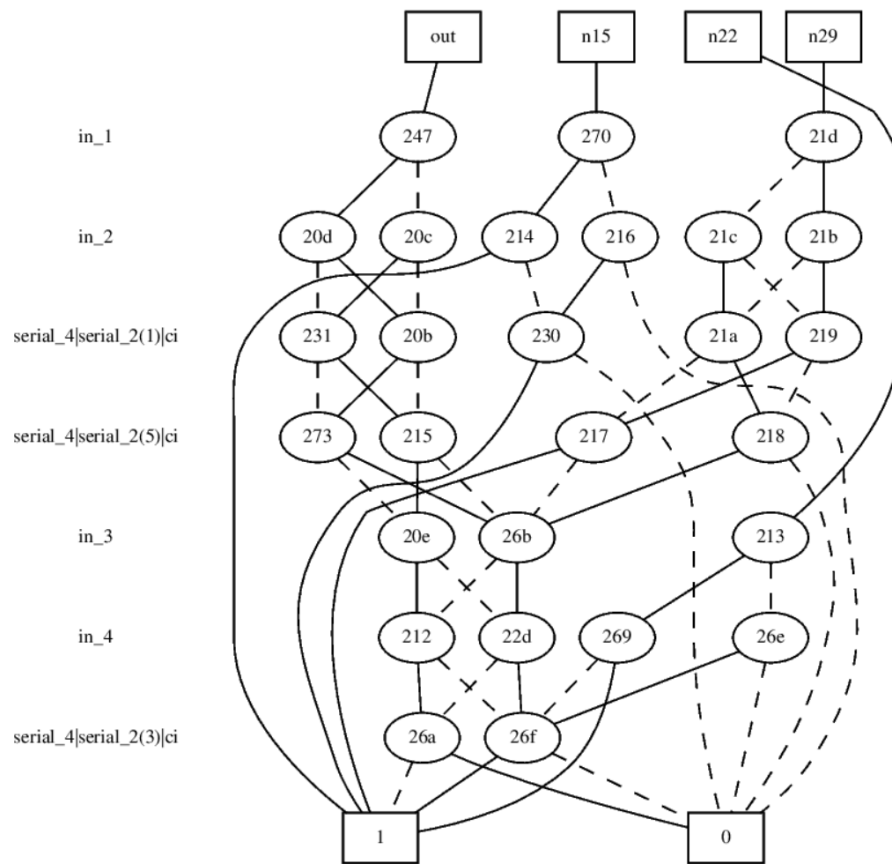


Figure 3: Step 7