

Department of Electrical Engineering, National Taiwan University

Figure 1: Results for Problem 1

One single command `logic` suffices.

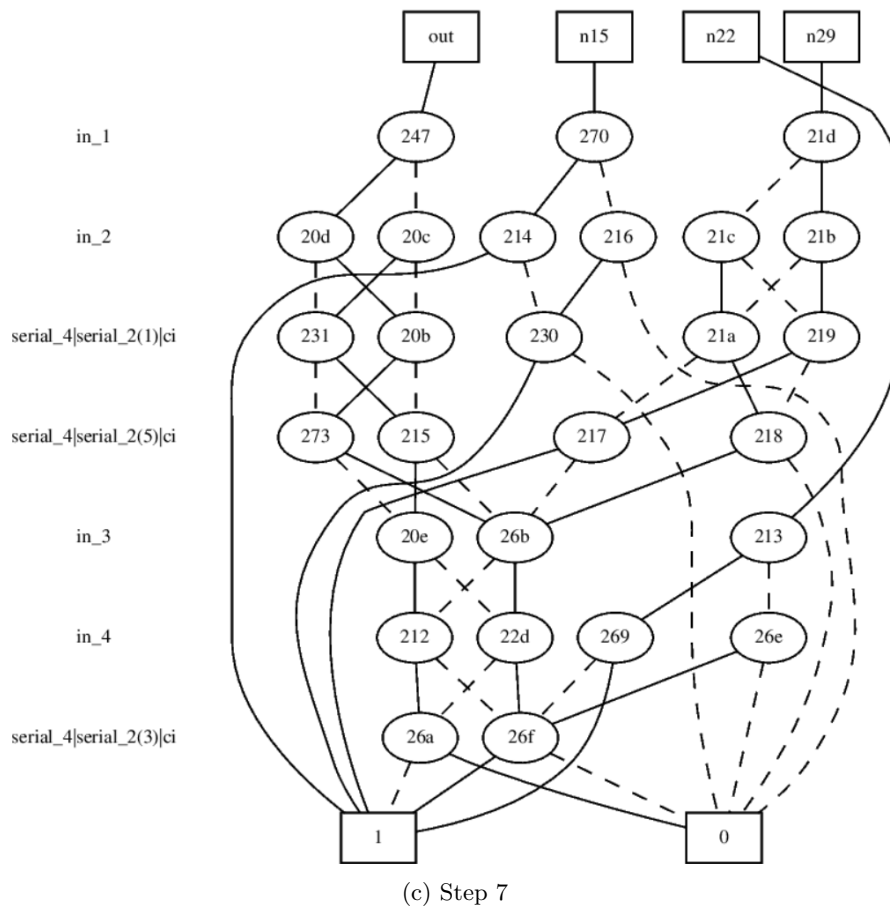
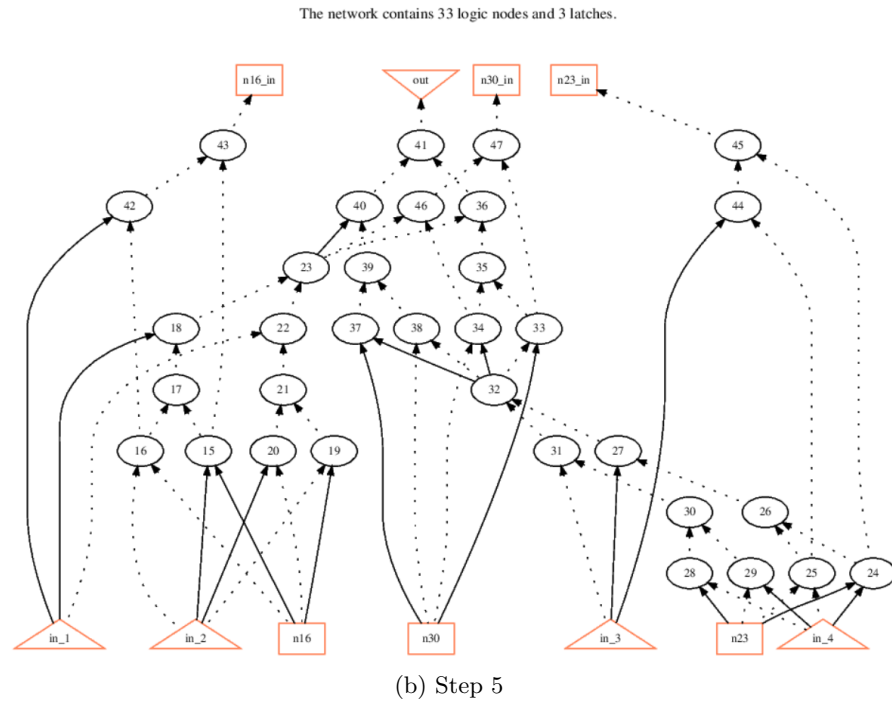


Figure 1: Results for Problem 1